



## Design Steps

1. Transfer function of this circuit:

$$V_o = (V_{i2} - V_{i1}) \times G + V_{ref}$$

When  $V_{ref} = 0$ , the transfer function simplifies to the following equation:

$$V_o = (V_{i2} - V_{i1}) \times G$$

$$\text{where } G = \frac{R_4}{R_3} \times 1 + \frac{2 \times R_5}{R_{10}}$$

2. Select the feedback loop resistors  $R_5$  and  $R_6$ :

Choose  $R_5 = R_6 = 10 \text{ k}\Omega$  (Standard Value)

3. Select  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ . To set the  $V_{ref}$  gain at  $1\text{V/V}$  and avoid degrading the instrumentation amplifier's CMRR, ratios of  $R_4/R_3$  and  $R_2/R_1$  must be equal.

Choose  $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$  (Standard Value)

4. Calculate  $R_{10}$  to meet the desired gain:

$$G = \frac{R_4}{R_3} \times \left( 1 + \frac{2 \times R_5}{R_{10}} \right) = 10 \frac{\text{V}}{\text{V}} \quad ( \quad )$$

$$R_4 = R_3 = 10 \text{ k}\Omega$$


$$\rightarrow G = 1 + \frac{2 \times 10 \text{ k}\Omega}{R_{10}} = 10 \frac{\text{V}}{\text{V}} \rightarrow 1 + \frac{20 \text{ k}\Omega}{R_{10}} = 10 \frac{\text{V}}{\text{V}}$$

$$\frac{20 \text{ k}\Omega}{R_{10}} = 9 \frac{\text{V}}{\text{V}} \rightarrow R_{10} = \frac{20 \text{ k}\Omega}{9} = 2222.2 \Omega \rightarrow R_{10} = 2.21 \text{ k}\Omega \text{ (Standard Value)} \quad (1)$$


5. To check the common-mode voltage range, download and install the program from reference [5]. Edit the INA\_Data.txt file in the installation directory by adding the code for a 3 op amp INA whose internal amplifiers have the common-mode range, output swing, and supply voltage range as defined by the amplifier of choice (TLV172 in this case). There is no  $V_{be}$  shift in this design and the gain of the output stage difference amplifier is  $1 \text{ V/V}$ . The default supply voltage and reference voltages are  $\pm 15 \text{ V}$  and  $0 \text{ V}$ , respectively. Run the program and set the gain and reference voltage accordingly. The resulting  $V_{CM}$  vs.  $V_{OUT}$  plot approximates the linear operating region of the discrete INA.

## Design Simulations

### DC Simulation Results

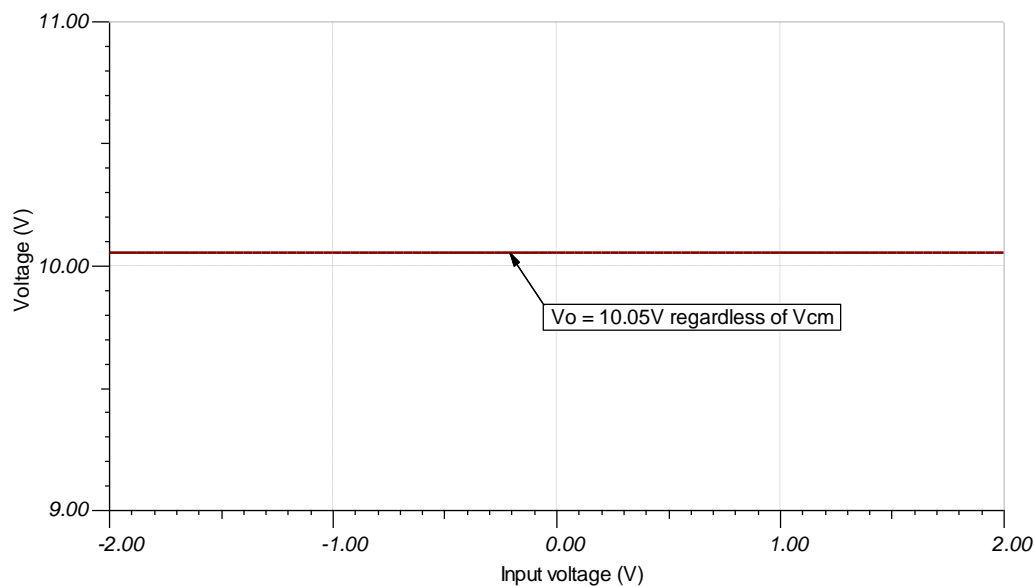

### Transient Simulation Results

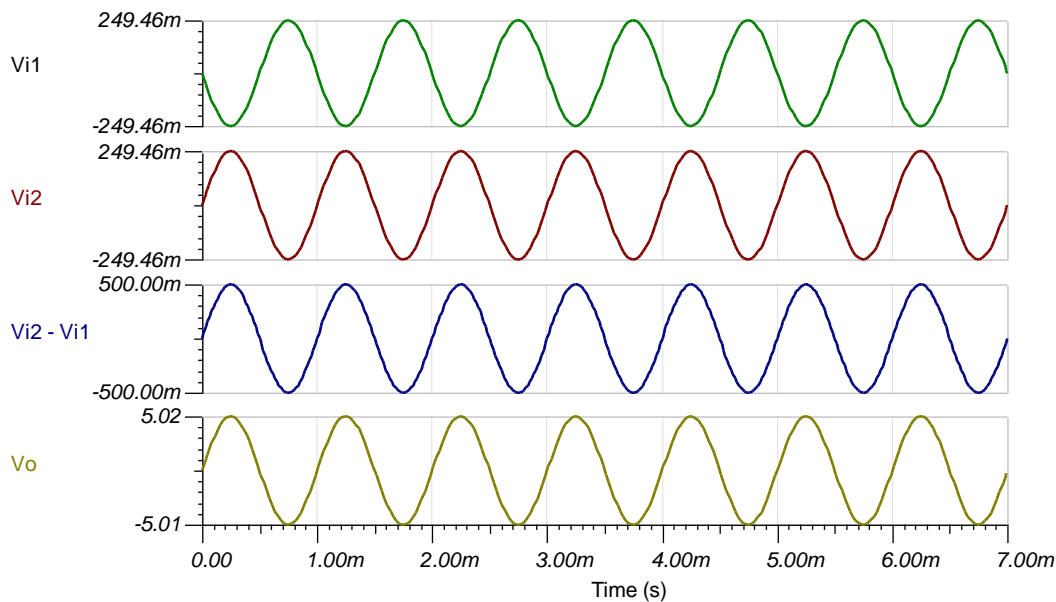

**References:**

1. [Analog Engineer's Circuit Cookbooks](#)
2. SPICE Simulation File [SBOMAU8](#)
3. [TI Precision Labs](#)
4. [Instrumentation Amplifier  \$V\_{CM}\$  vs.  \$V\_{OUT}\$  Plots](#)
5. [Common-mode Range Calculator for Instrumentation Amplifiers](#)

**Design Featured Op Amp**

TLV171	
$V_{SS}$	4.5V to 36V
$V_{inCM}$	$(V-) - 0.1V < V_{in} < (V+) - 2V$
$V_{out}$	Rail-to-rail
$V_{os}$	0.25mV
$I_q$	475 $\mu$ A
$I_b$	8pA
UGBW	3MHz
SR	1.5V/ $\mu$ s
#Channels	1,2,4
<a href="http://www.ti.com/product/tlv171">www.ti.com/product/tlv171</a>	

**Design Alternate Op Amp**

	OPA172	OPA192
$V_{SS}$	4.5V to 36V	4.5V to 36V
$V_{inCM}$	$(V-) - 0.1V < V_{in} < (V+) - 2V$	$V_{ee} - 0.1V$ to $V_{cc} + 0.1V$
$V_{out}$	Rail-to-rail	Rail-to-rail
$V_{os}$	0.2mV	$\pm 5\mu$ V
$I_q$	1.6mA	1mA/Ch
$I_b$	8pA	5pA
UGBW	10MHz	10MHz
SR	10V/ $\mu$ s	20V/ $\mu$ s
#Channels	1,2,4	1, 2, 4
	<a href="http://www.ti.com/product/opa172">www.ti.com/product/opa172</a>	<a href="http://www.ti.com/product/opa192">www.ti.com/product/opa192</a>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated