

# EE230: Lab-7

## Active Filters

Prateek Garg, 20D070060

March 13, 2022


## 1 Overview of the experiment

### 1.1 Aim of the experiment


The aim of the experiment is to create Active filter circuits using opamp LM741 and plot gain vs frequency. g the values to a python script to plot them using Matplotlib.

## 2 Design

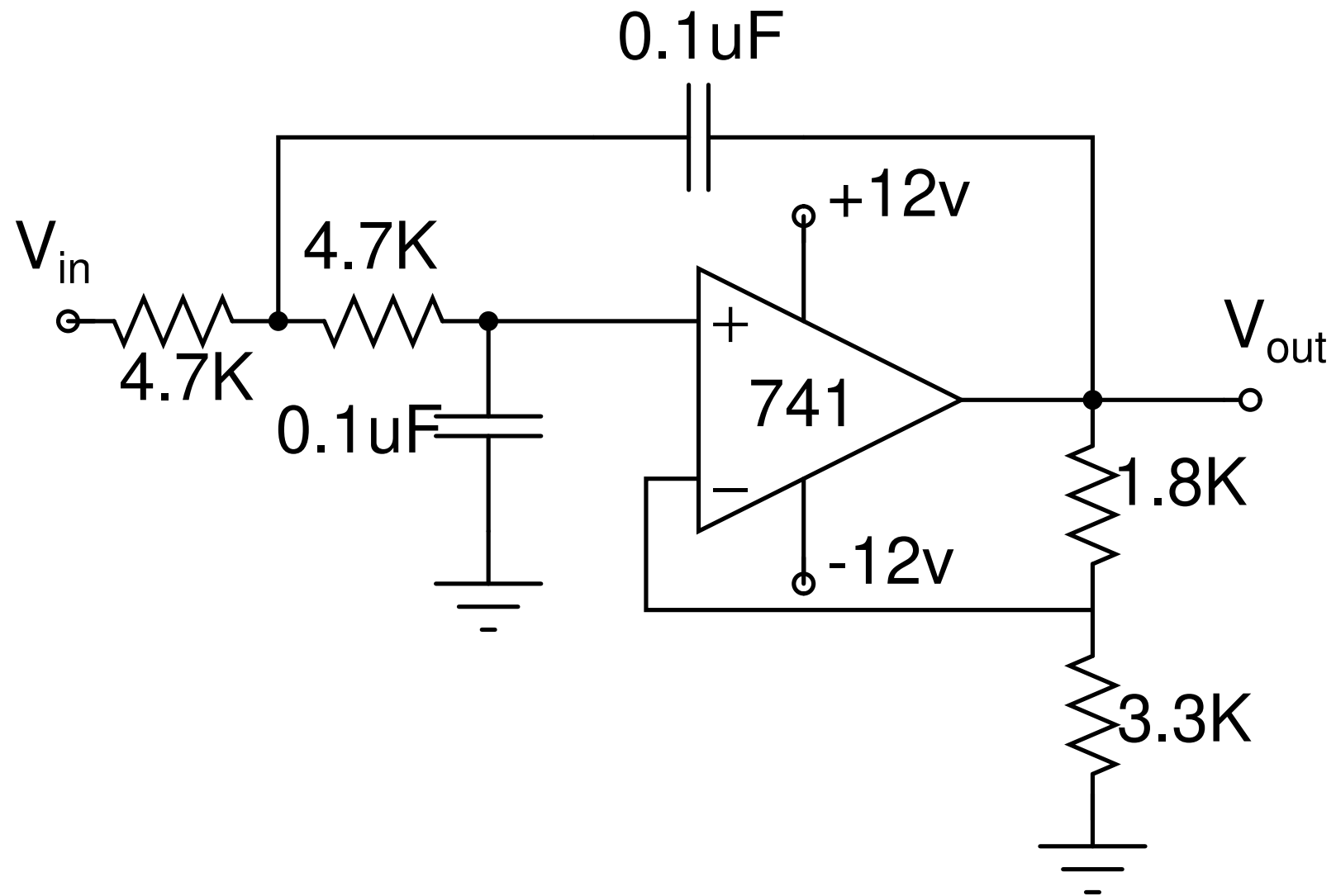
### 2.1 Sallen-Key Active Low-Pass Filter


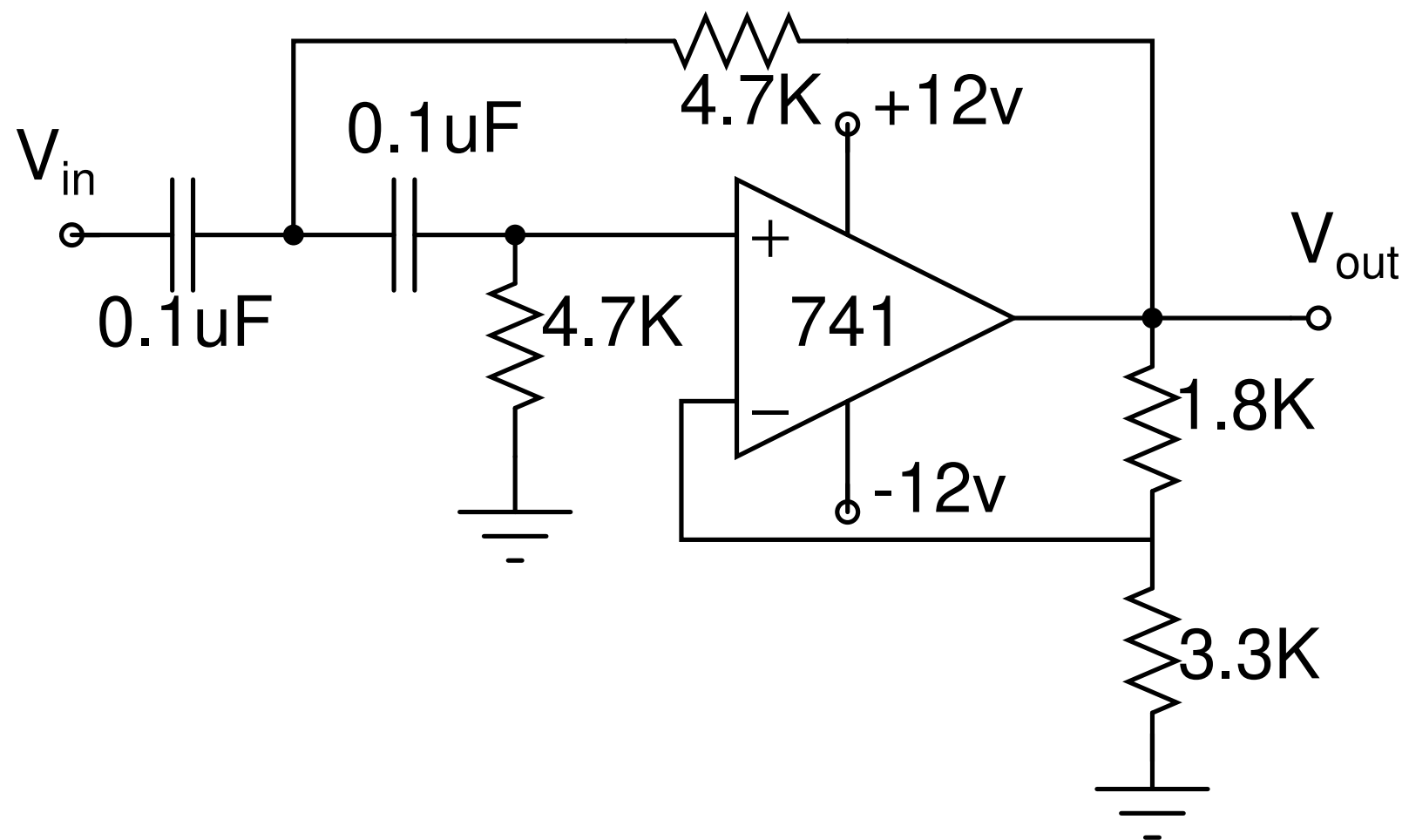
## 2.2 Sallen-Key Active High-Pass Filter



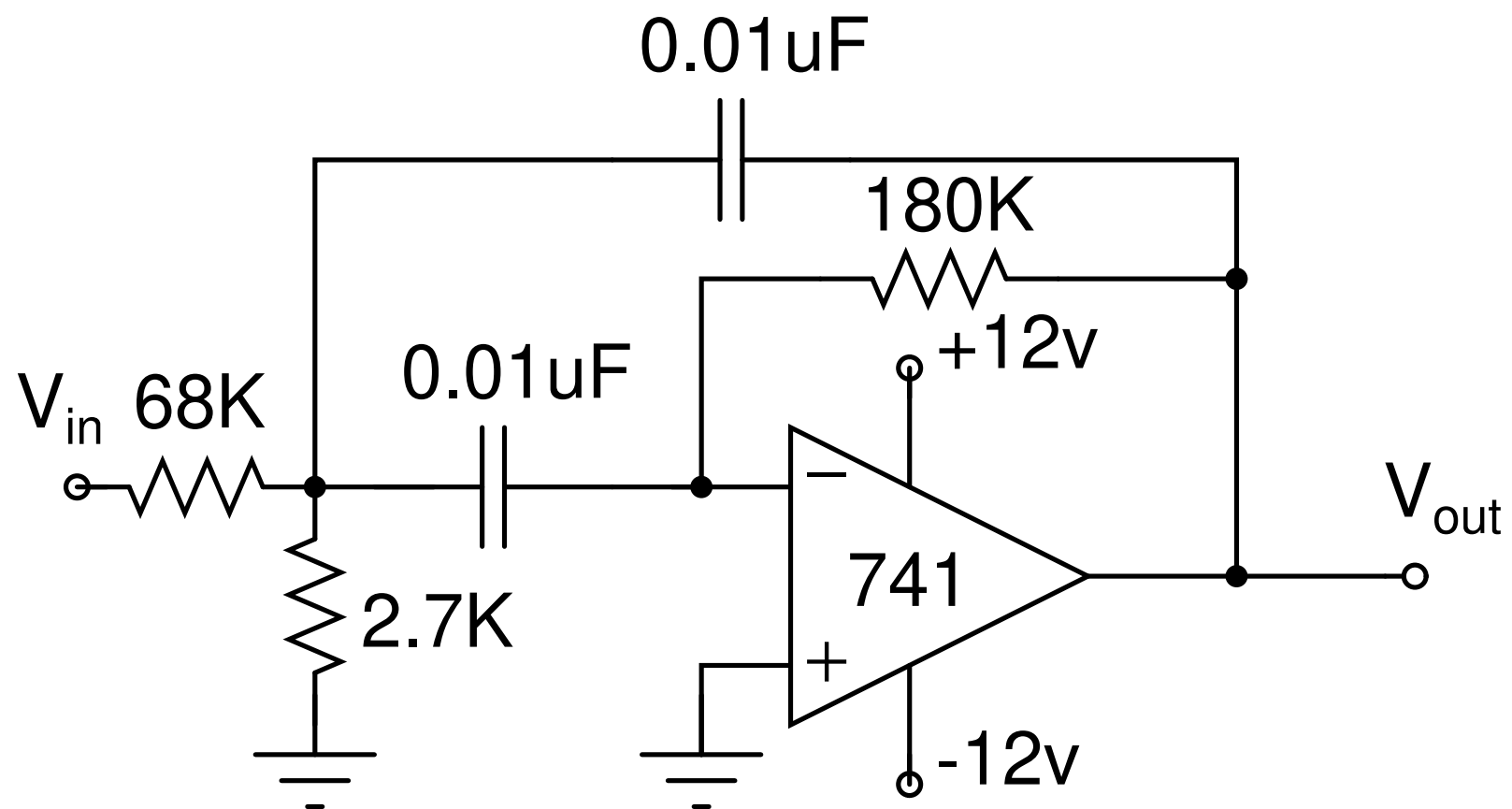
### 2.3 Multiple-feedback Active Bandpass Filter



### 3 Experimental results


#### 3.1 Sallen-Key Active Low-Pass Filter

Gain(db) vs. f

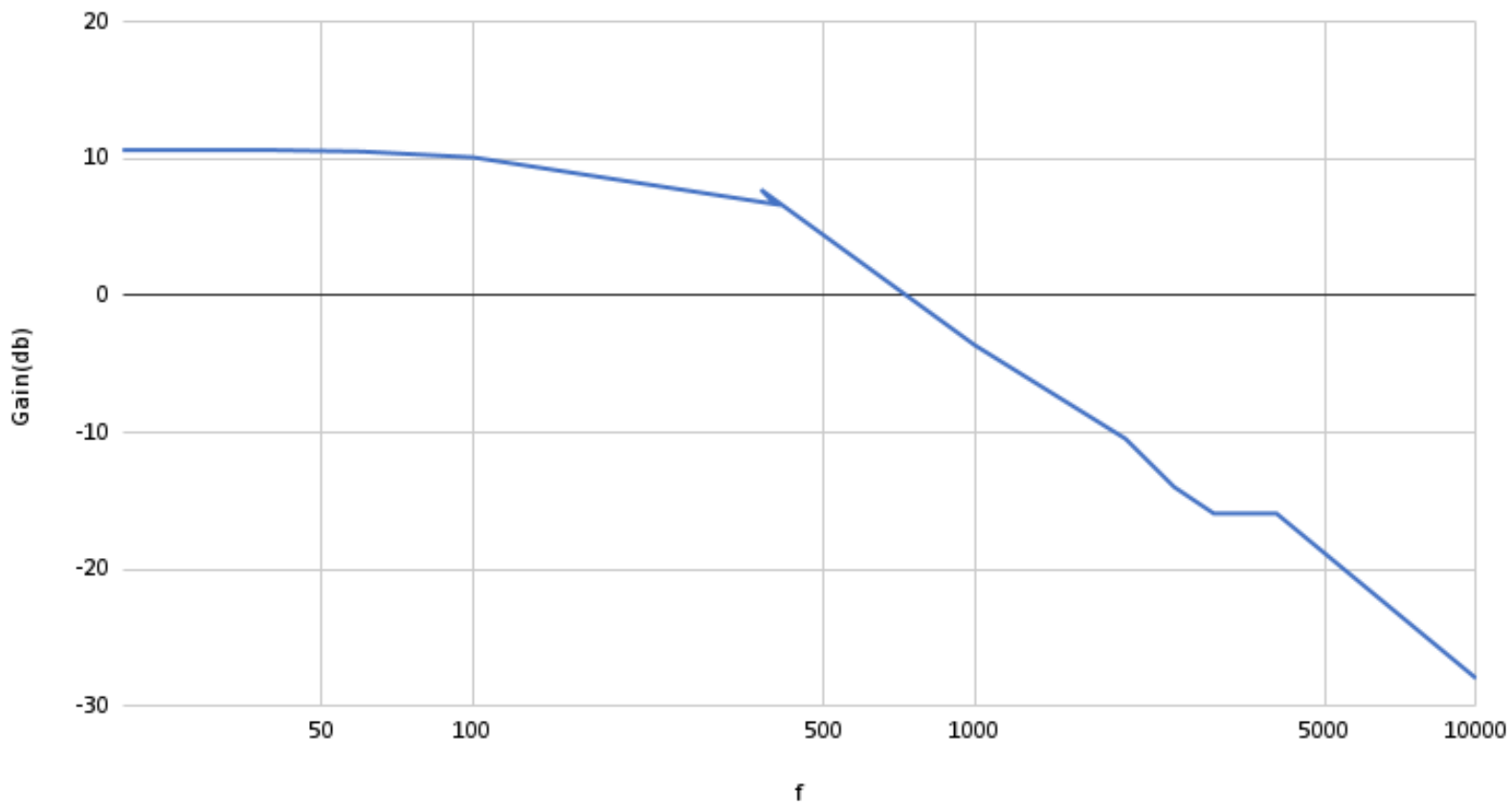


Theoretical Cut-off frequency=338.62Hz Experimental Cut-off frequency=375Hz  
Roll-off=-22.6 Experimental Values quite match the theoretical Expectations.
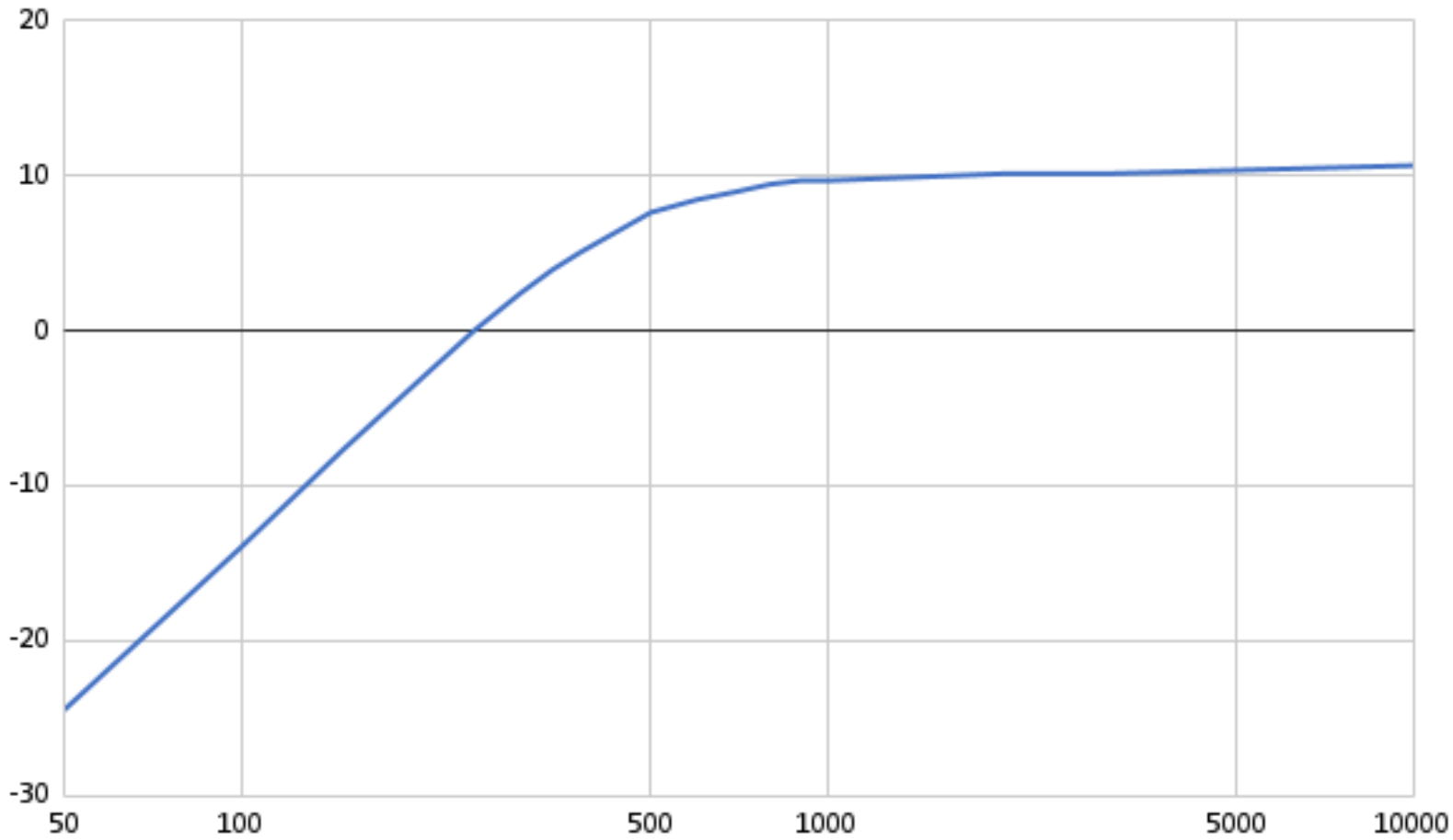
### 3.2 Sallen-Key Active High-Pass Filter



Theoretical Cut-off frequency=338.62Hz Experimental Cut-off frequency=400Hz  
Roll-off=36.124 Experimental Values quite match the theoretical Expectations.
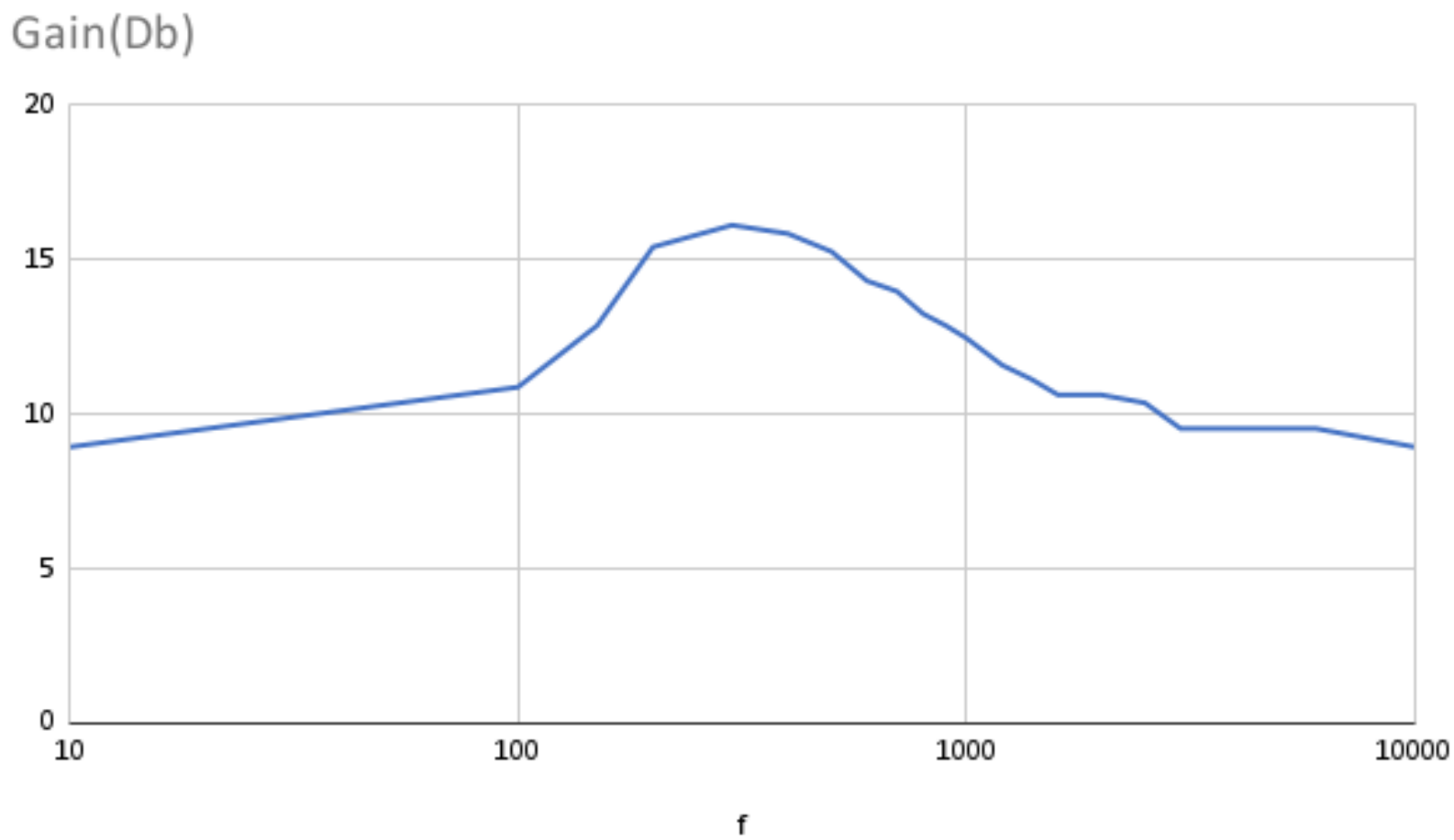
### 3.3 Multiple-feedback Active Bandpass Filter



## 4 Experiment completion status

All the sections were completed