

# EE230: Experiment No.8

## Logarithmic Amplifier

Prateek Garg, 20D070060

March 21, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

The aim of this experiment is to understand Logarithmic Amplifier using op-amps (specifically TL084) about how it works and should be the circuit to implement this type of Amplifier. In this experiment, we have to find the linear region at which we can use the given circuit for our use, given the IV characteristics of the circuit. This circuit is simulated using NgSpice software, and these simulation results needs to be compared with the theoritical results.

### 1.2 Methods


First of all, the given IV characteristics are analyzed, we find the linear region to work upon the om-amp, and by using linear regression in python, we find the slope and the y-intercept (which is required for further calculations).

After that, circuit diagrams are made using XCCircuit software of the required circuits. Now, as the circuits are formed, netlist codes are written for the circuit to completely describe the circuit and also describe what result ngspice should show to us. The readings are saved in a file and then, using this file, plots of the given parameters are made by matplotlib python script.

The lab work to be done was given in lab pdf, using that we got the circuit to be simulated.

After that, these plots were compared with the theoritical plot values and the changes are done to the circuit element values to refine the circuit.

## 2 Design

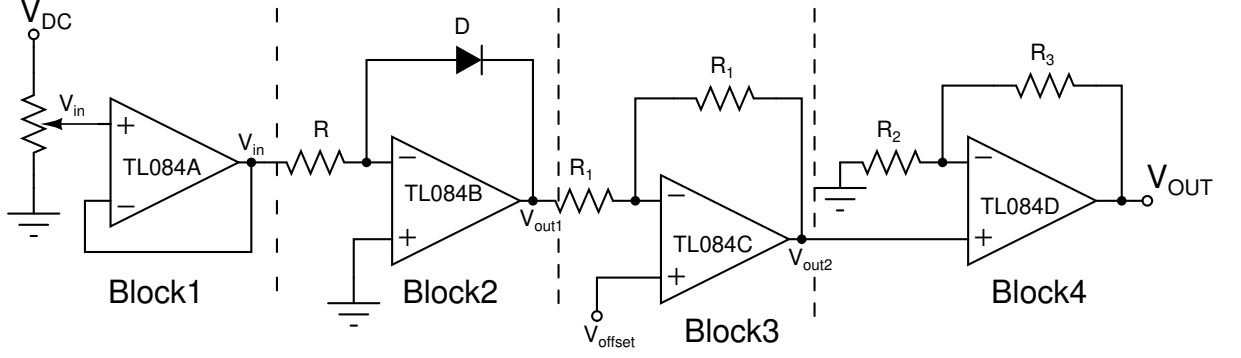

The equation for the terminal characteristics of a pn junction diode in forward bias is

$$I_D = I_S * e^{(V_D/nV_T)} \quad (1)$$

$$V_D = nV_T(\ln(I_D) - \ln(I_S)) \quad (2)$$

$$\ln(I_D) = V_D/nV_T + \ln(I_S) \quad (3)$$

$$V_{out1} = -V_D \quad (4)$$

$$V_{out1} = nV_T(\ln(I_S R) - \ln(V_{in})) \quad (5)$$

$$V_{out1} = a_1 \ln(V_{in}) + a_2 \quad (6)$$

$$a_1 = -nV_T \quad (7)$$

$$a_2 = nV_T \ln(I_S R) \quad (8)$$

We can remove the offset by subtracting  $a_2$  from  $V_{out1}$ . The result can then be multiplied by  $1/a_1$  using a suitable amplifier, to obtain at the output the true natural logarithm of  $V_{in}$ .

The third block is used for removing the offset from  $V_{out1}$ , set  $V_{offset} = a_2/2$ , so the input to block 4 would be  $-a_1 \ln(V_{in})$ .

$$V_{out} = -a_1(1 + R_3/R_2)\ln(V_{in}) \quad (9)$$

Choosing  $1 + R_3/R_2 = -1/a_1$ , we get

$$V_{out} = \ln(V_{in}) \quad (10)$$

The role of block 1 is to avoid loading the source of  $V_{in}$  by block 2.

If we assume that the maximum input voltage,  $V_{in2} = 10V$ , then  $R = 10/I_{D2}$ .

**Values:-**

By observing the readings, we got linear region  $I_D$  values from 1.266E-4 to 5.55E-4 Amperes.

So,

$$R = 10/I_{D2} = 18k\Omega \quad (11)$$

By using linear regression in this region, we got slope = 20.5409, and y-intercept = -19.30584.

$$Slope = 1/(nV_T) \quad (12)$$

$$Y - intercept = \ln(I_S) \quad (13)$$

$$n = 1/(slope * V_T) = 1.87 \quad (14)$$

$$I_S = e^{(y-intercept)} = 4.13nA \quad (15)$$

$$a_1 = -(1.87)(26)/1000 = -0.04862 \quad (16)$$

$$a_2 = (1.87)(26)\ln(4.13 * 18/1000000)/1000 = -0.46 \quad (17)$$

$$V_{offset} = a_2/2 = (nV_T\ln(I_S R))/2 = -0.23V \quad (18)$$

We set  $R_1 = 10k\Omega$ .

$$R_3/R_2 = (-1/a_1) - 1 = 19.5 \quad (19)$$

We set  $R_2 = 1k\Omega$ , and  $R_3 = 19.5k\Omega$ .

Now, we are done with all the calculations for finding the values of all the required values and parameters.

## 3 Simulation results

### 3.1 Code snippet

#### Logarithmic Amplifier

```

1 Logarithmic Amplifier
2
3 .include 1N4148_1.txt
4 .include TL084.TXT
5 *describe circuit
6 * <element-name> <nodes> <value/nodel>
7
8 Vin 11 0 dc 0
9 x1 11 15 3 4 15 TL084
10 *-----
11 R6 15 22 1455.60
12 D1 22 25 1N4148
13 x2 0 22 3 4 25 TL084
14 *-----
15 R1 25 32 100
16 R12 35 32 100
17 x3 31 32 3 4 35 TL084
18 Voff 31 0 -0.293
19 *-----
20 R2 42 0 100
21 R3 42 45 1892
22 x4 35 42 3 4 45 TL084
23 *-----
24 vcc 3 0 dc 15v
25 vee 4 0 dc -15v
26
27 .dc Vin 0 10 0.1
28 *analysis command
29
30 .control
31 run
32
33 *display cmd
34 plot v(45) v(11)
35 print v(45) v(11)
36 *end control mode
37 .endc
38
39 *end netlist
40 .end

```

### 3.2 Simulation results

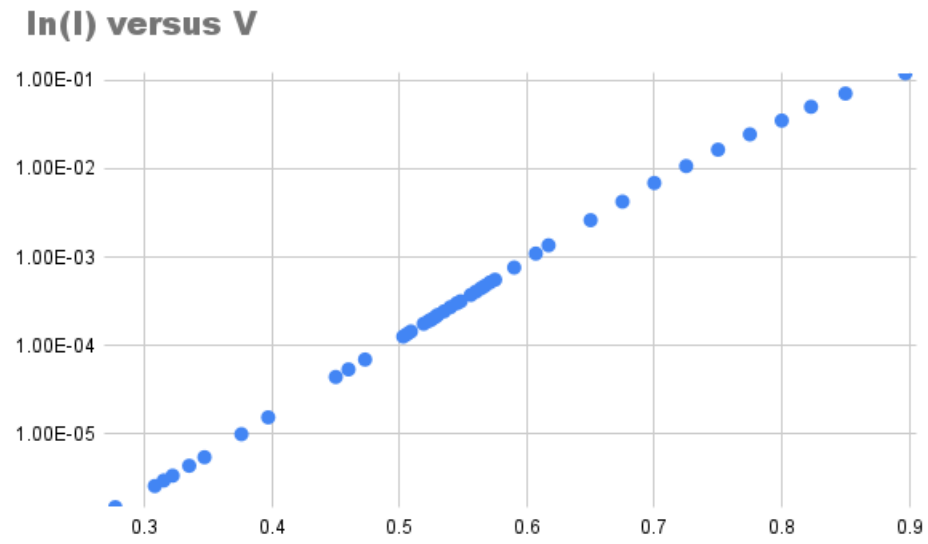


Figure 1: IV characteristics from the given data

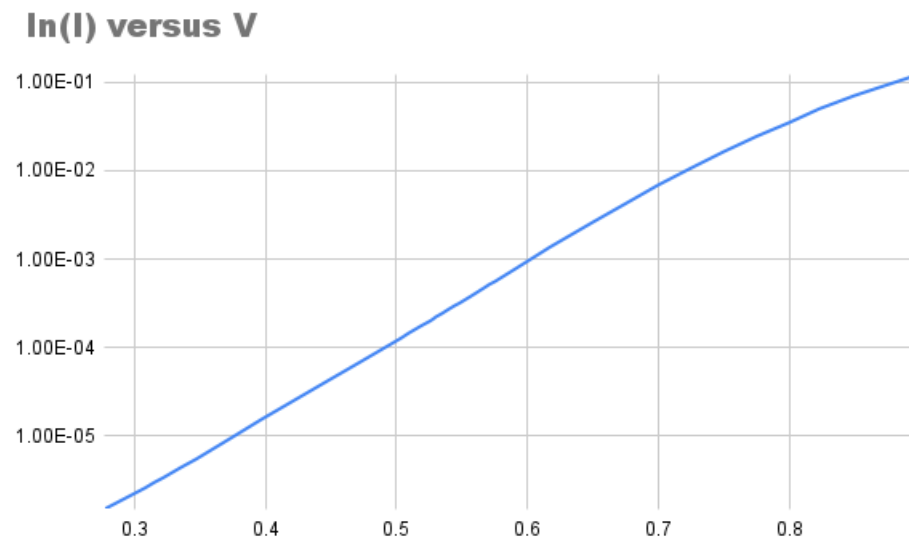


Figure 2:  $V_{out}$  vs  $\ln(V_{in})$  Curve fitting

### Vout vs Vin

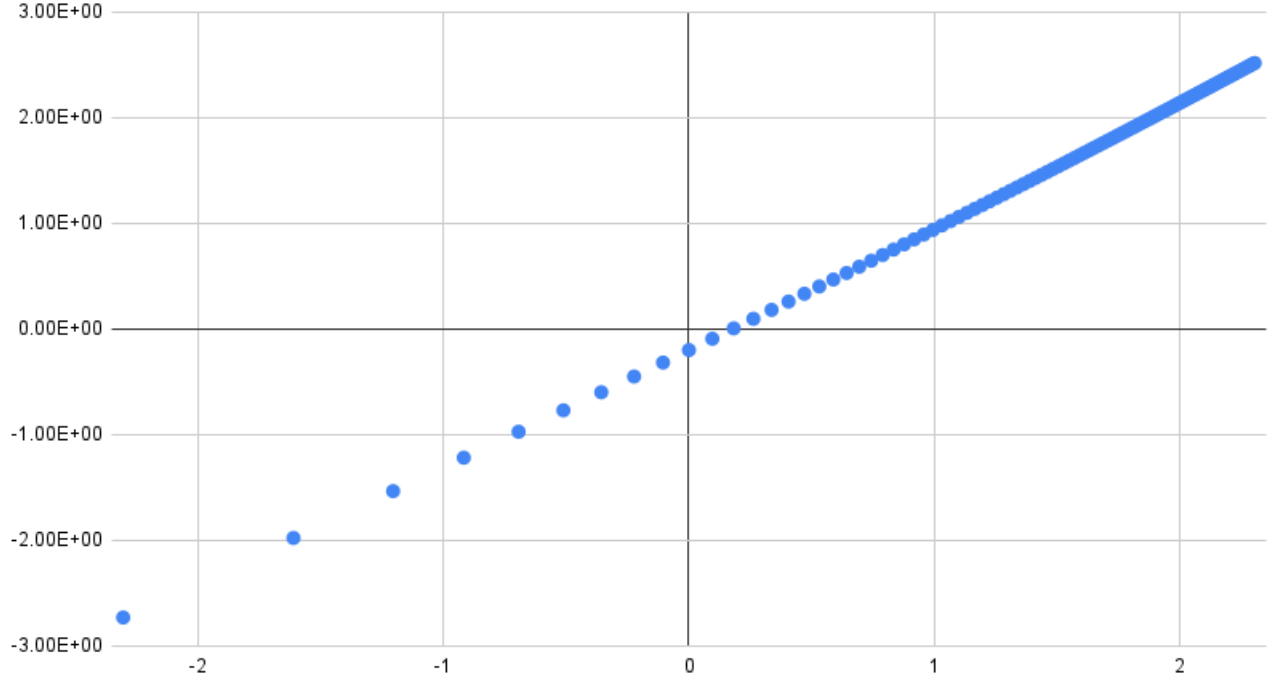


Figure 3:  $V_{out}$  vs  $\ln(V_{in})$  Experimental

## 4 Experimental results

Our value of  $V_{offset}$ , which came from the experimental IV data is -0.23V. But to make the  $V_{out}$  vs  $\ln(V_{in})$  graph to pass through (0,0), we have to make the  $V_{offset} = -0.219V$ .

To make the slope of this graph as 1, we had to change the value of  $R_2$  from  $1k\Omega$  (came by experimental analysis), to  $1.1k\Omega$ .

So, because of changing  $V_{offset}$  from -0.23V to -0.219V,  $a_2$  value changes from -0.46 to -0.438.

Due to changing of  $R_2$  from 1k to 1.1k,  $a_1$  value changes from -0.04862 to -0.05344.

## 5 Experiment completion status

All the parts of this experiment are completed successfully.