

EE230: Lab-3

Precision Rectifier using Opamp

Prateek Garg, 20D070060

January 28, 2022

1 Overview of the experiment

1.1 Aim of the experiment

The aim of the experiment is to create a improved design of Hal-wave and full-wave rectifiers using Opamps and then simulate the designs in ngspice.

1.2 Methods

1.2.1 Half-wave Precision Rectifier

We use the opamp circuit file `ua741.txt` and `Diode_1N914.txt` file for Diode circuit. Using two different diode configurations we make two Half-Wave rectifier circuits working on alternate cycles of inputs


1.2.2 Full-wave Precision Rectifier

We use the opamp circuit file `ua741.txt` and `Diode_1N914.txt` file for Diode circuit. We start by defining subcircuits for Half-Wave rectifier and another subcircuit for Inverting-Summer. Then the netlist was used to describe connections.


All the designs were simulated on Ngspice and exporting the values to a python script to plot them using Matplotlib.

2 Design


2.1 Half Wave Rectifier A

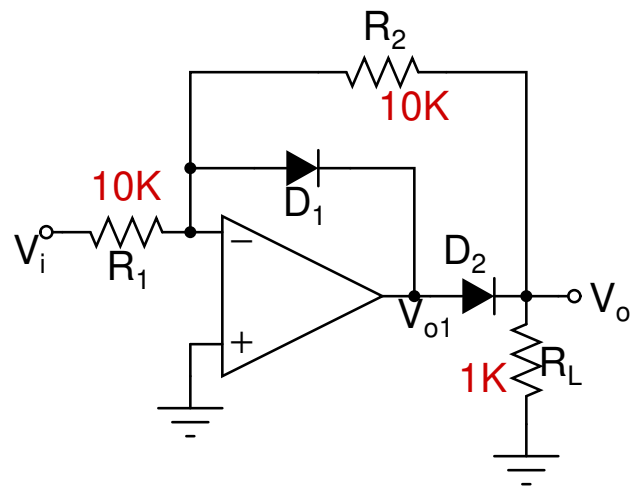

2.2 Half Wave Rectifier B

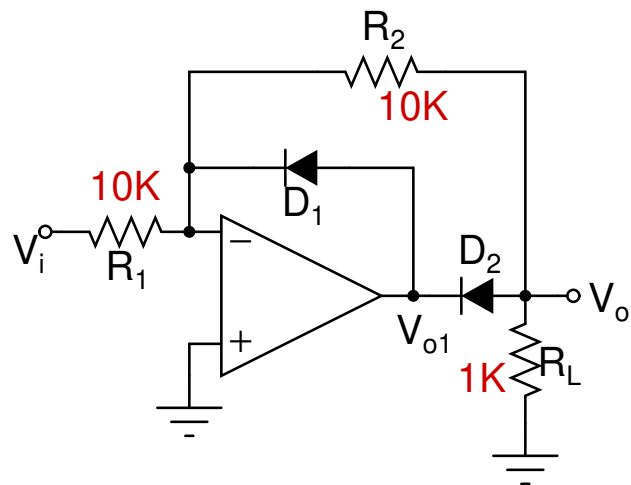

2.3 Full Wave Rectifier

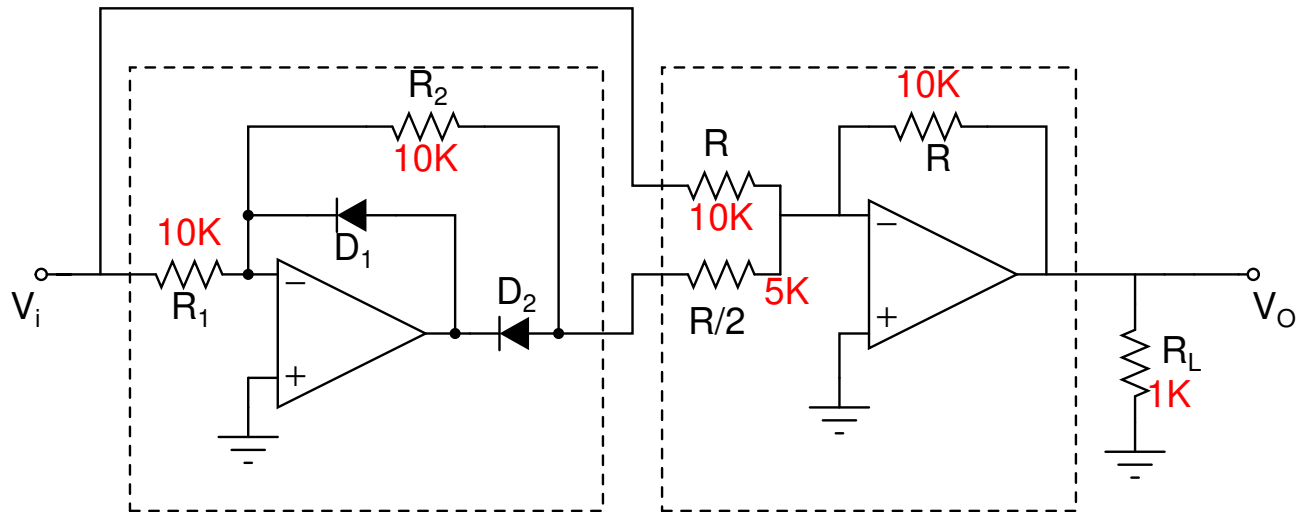

3 Simulation results

3.1 Half Wave Rectifier A

3.1.1 Code snippet

```

1 Improved-Half-Wave-Rectifier-A
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include Diode_1N914.txt
5 *Connections as mentioned in subcircuit file
6 x1 0 1 2 3 6 UA741
7 d1 6 4 1N914
8 d2 1 6 1N914
9 r1 5 1 10k
10 r2 4 1 10k
11 rl 4 0 1k
12 vcc 2 0 dc 15v
13 vee 3 0 dc -15v
14 vin 5 0 sin (0 5 1k 0 0)
15 .tran 0.02ms 6ms
16 .control
17 run


```

```

18 plot v(4) v(6) v(5)
19 print v(4) v(6) v(5)
20 .endc
21 .end

```

3.1.2 Simulation results

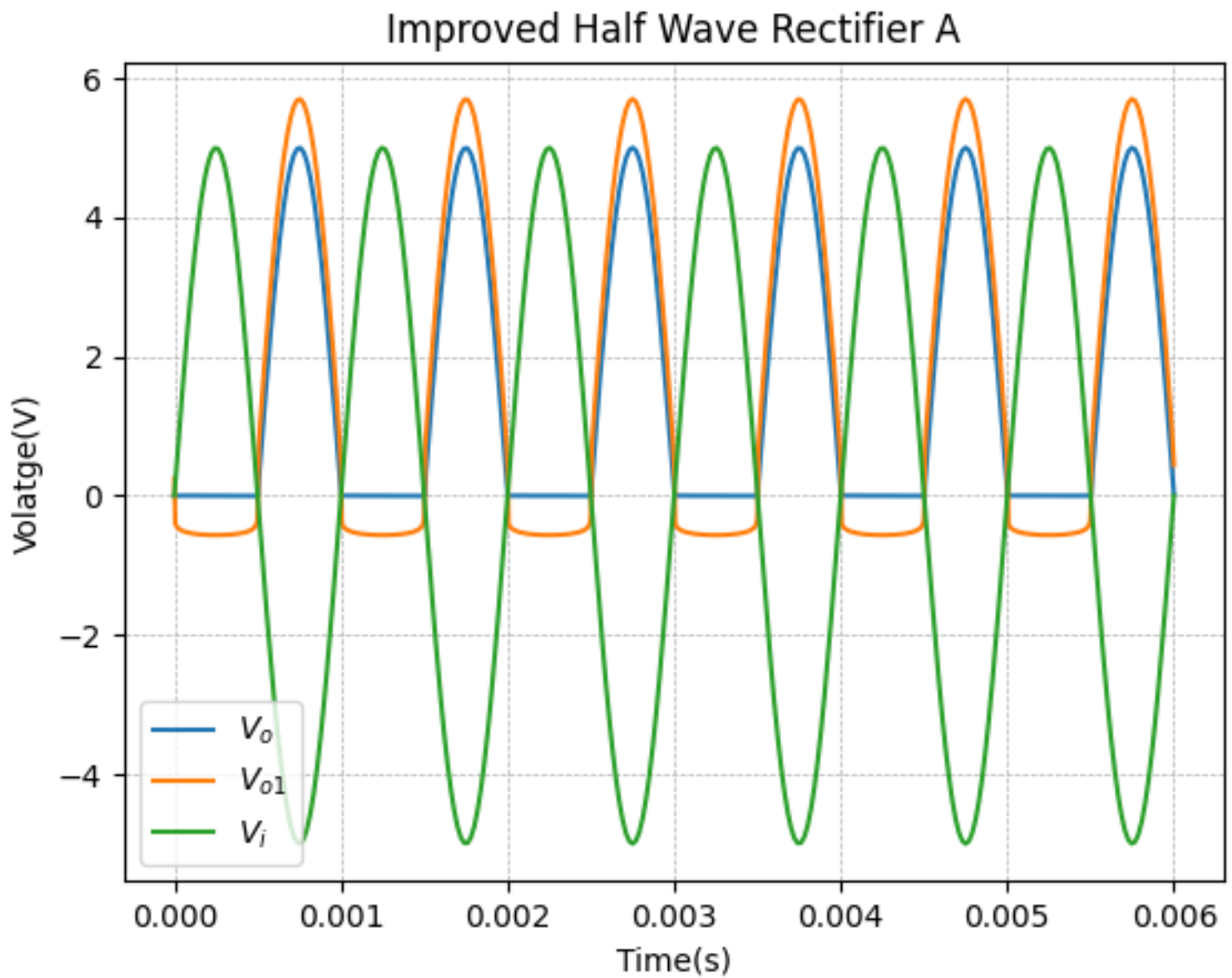


3.2 Half Wave Rectifier B

3.2.1 Code snippet

```
1 Improved-Half-Wave-Rectifier-B
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include Diode_1N914.txt
5 *Connections as mentioned in subcircuit file
6 x1 0 1 2 3 6 UA741
7 d1 4 6 1N914
8 d2 6 1 1N914
9 r1 5 1 10k
10 r2 4 1 10k
11 rl 4 0 1k
12 vcc 2 0 dc 15v
13 vee 3 0 dc -15v
14 vin 5 0 sin (0 5 1k 0 0)
15 .tran 0.02ms 6ms
16 .control
17 run
18 plot v(4) v(6) v(5)
19 print v(4) v(6) v(5)
20 .endc
```

3.2.2 Simulation results

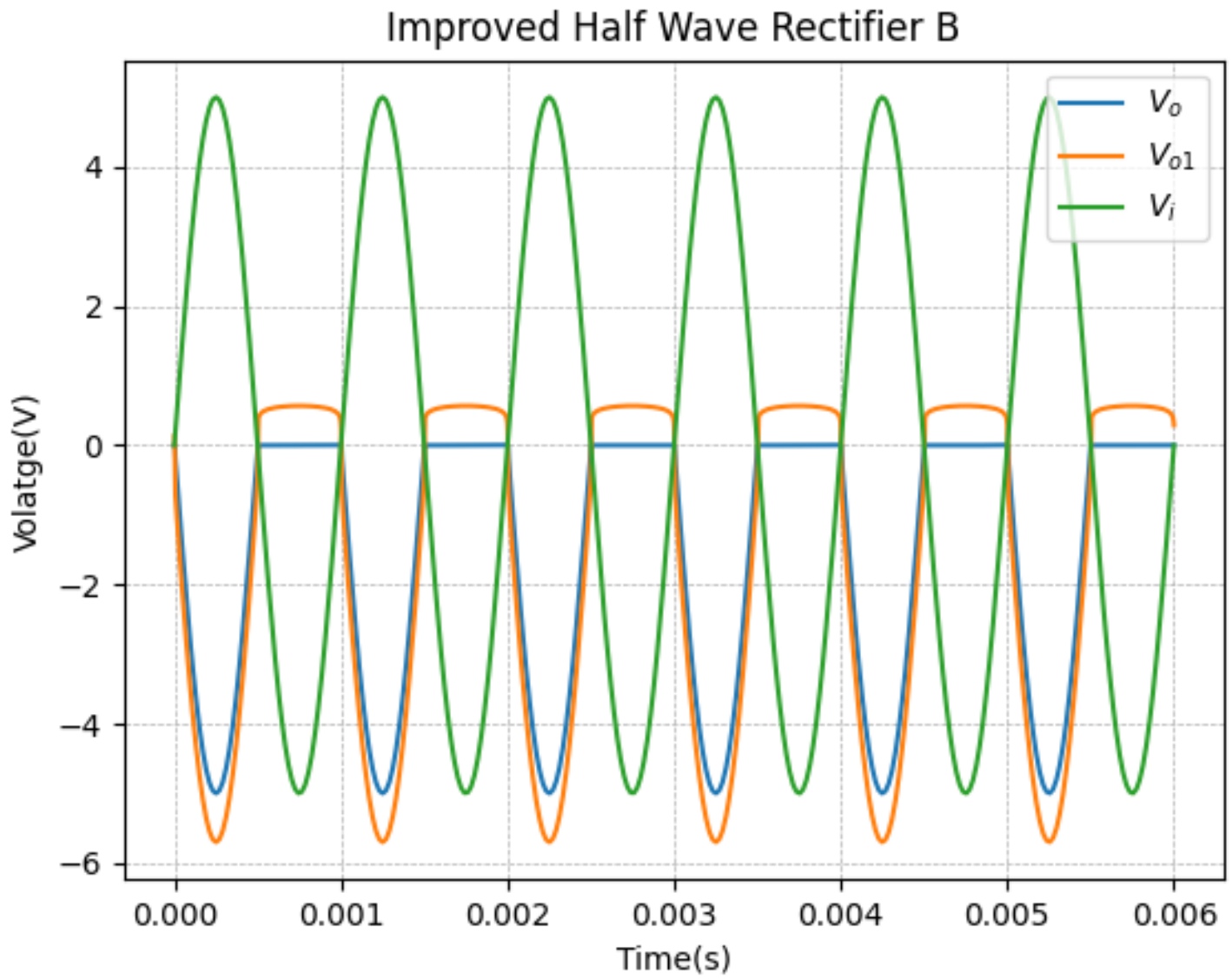

3.3 Full Wave Rectifier


3.3.1 Code snippet

```

1 Improved-Half-Wave-Rectifier-A
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include Diode_1N914.txt
5 *Connections as mentioned in subcircuit file
6
7 .subckt Improved_Half_Wave_Rectifier_B In Out com
8 x1 com 1 2 3 6 UA741
9 d1 Out 6 1N914
10 d2 6 1 1N914
11 r1 IN 1 10k
12 r2 Out 1 10k
13 r1 Out com 1k
14 vcc 2 com dc 15v
15 vee 3 com dc -15v
16 .ends
17
18 .subckt Inverting_summer In1 In2 Out com
19 x1 com 1 2 3 Out UA741
20 r1 IN1 1 10k
21 r2 IN2 1 5k
22 r3 1 Out 10k
23 vcc 2 com dc 15v
24 vee 3 com dc -15v
25 .ends
26
27 xhw 1 2 0 Improved_Half_Wave_Rectifier_B
28 xis 1 2 3 0 Inverting_summer
29 vin 1 0 sin (0 5 1k 0 0)
30 Rl 3 0 1k
31 .tran 0.02ms 6ms
32 .control
33 run
34 plot v(3) v(1)
35 print v(1) v(3)
36 .endc


```

3.3.2 Simulation results

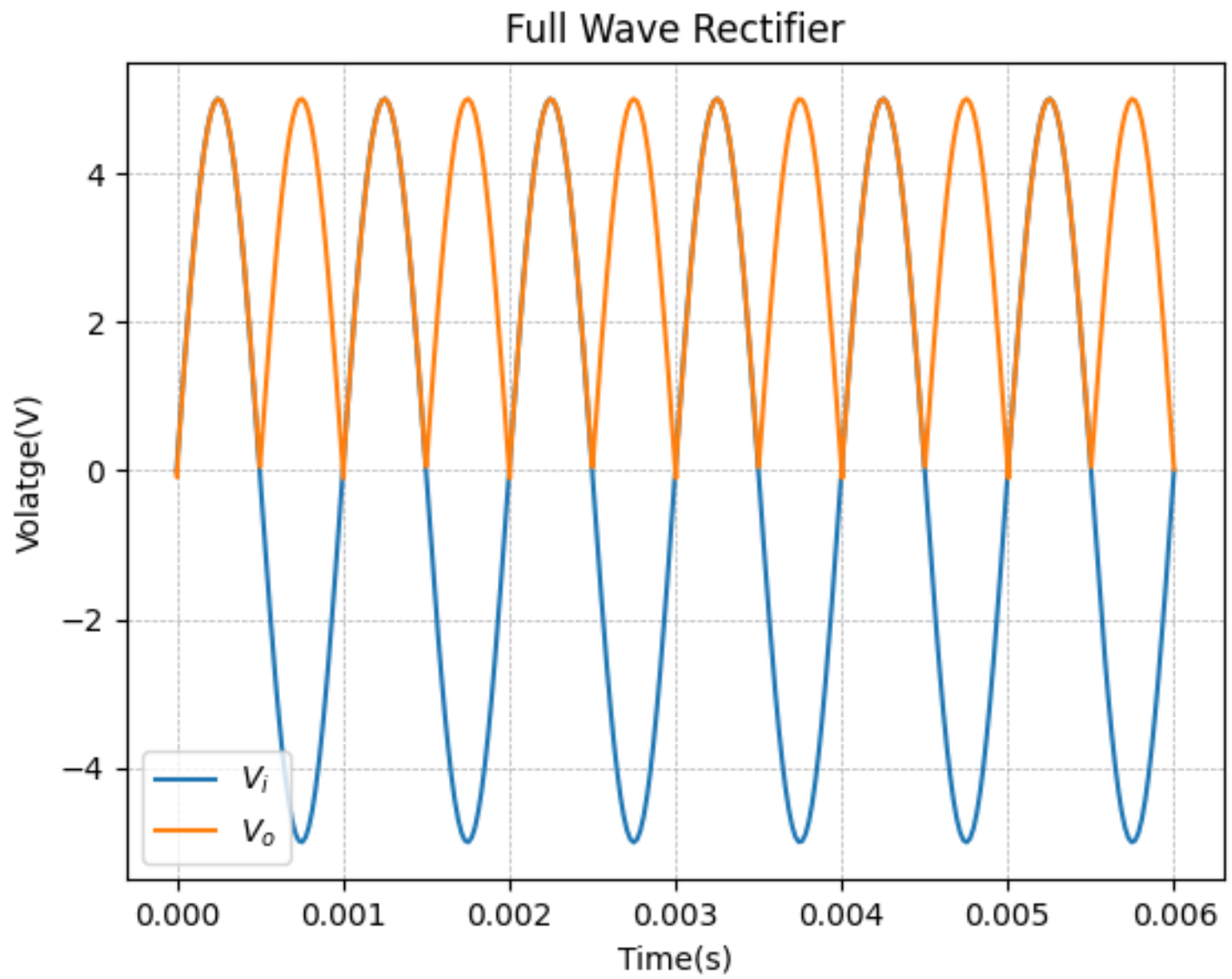


4 Experimental results

4.1 Half Wave Rectifier A

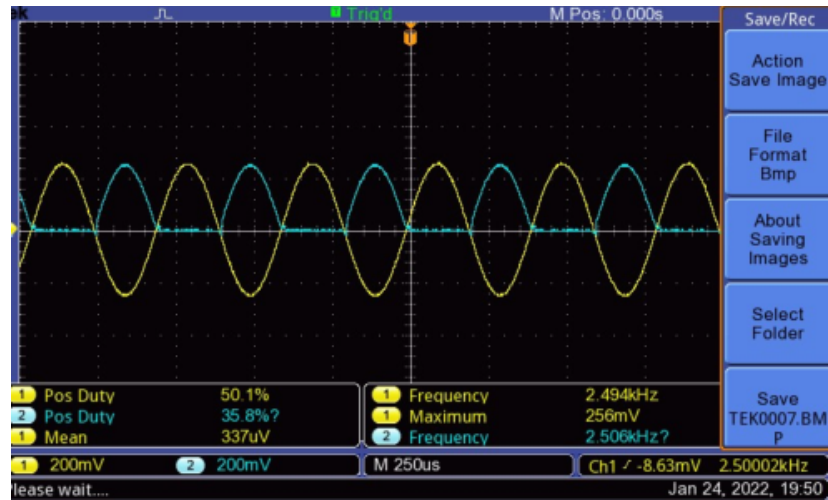


The experimental results match theoretical predictions quite well.

4.2 Half Wave Rectifier B

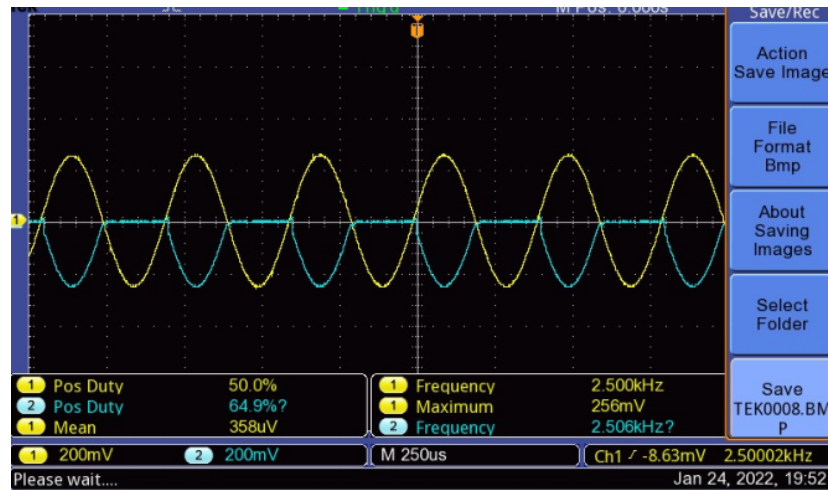

The experimental results match theoretical predictions quite well.

4.3 Full Wave Rectifier

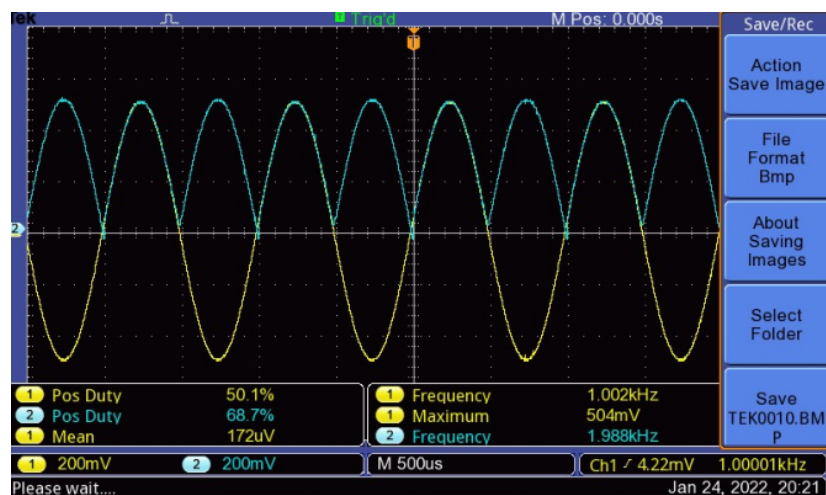

The experimental results match theoretical predictions quite well.

5 Experiment completion status

All the sections were completed