

EE230: Lab-3

Circuits using OP-AMPS

Prateek Garg, 20D070060

February 6, 2022

1 Overview of the experiment

1.1 Aim of the experiment

The aim of the experiment is to study and simulate various opamp circuits in ngspice namely:


1. Schmidt Trigger
2. Astable Multivibrator
3. Monostable Multivibrator

1.2 Methods


We start by analysing the circuits and then simulating in ngspice to check against theoretical expectations.

2 Design


2.1 Schmidt Trigger

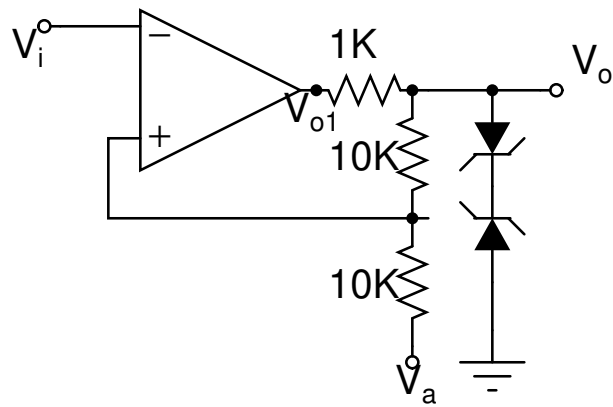

2.2 Astable Multivibrator

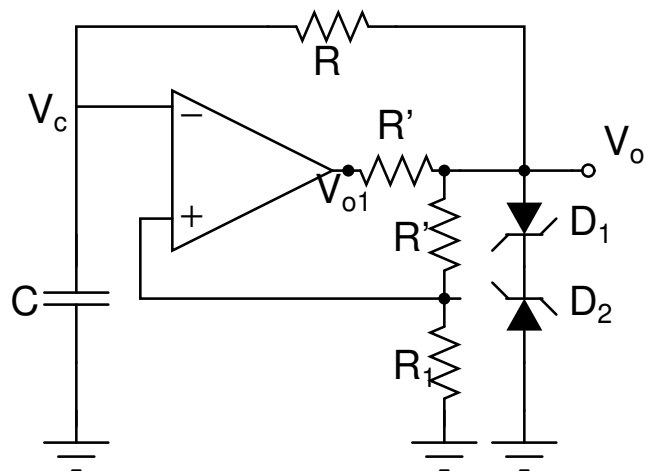

2.3 Monostable Multivibrator

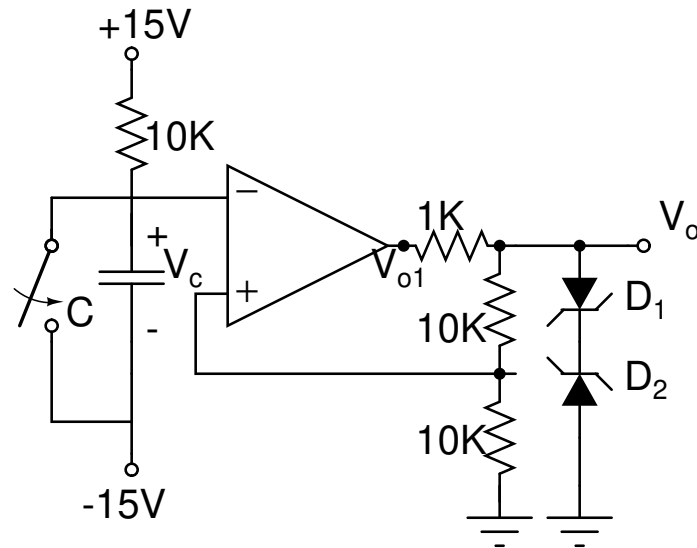

3 Simulation results

3.1 Schimdt Trigger

3.1.1 Code snippet

```

1 Schmitt trigger
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include zener_B.txt
5
6 .SUBCKT ZENER_12 1 2
7 D1 1 2 DF
8 DZ 3 1 DR
9 VZ 2 3 3.48
10 .MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p VJ=1.00 M
    =0.330
11 + TT=50.1n)
12 .MODEL DR D ( IS=5.49f RS=50 N=1.77 )
13 .ENDS
14
15 *Connections as mentioned in subcircuit file

```

```

16 x1 2 9 3 4 5 UA741
17 R1 2 6 10K
18 R2 2 7 10K
19 R3 5 7 1K
20 xz1 8 7 ZENER_12
21 xz2 8 0 ZENER_12
22 vcc 3 0 dc 15v
23 vee 4 0 dc -15v
24
25 va 6 0 dc 3
26 vin 9 0 sin(0 6 1k 0 0)
27 .tran 0.001m 0.01
28 .control
29 run
30 plot v(7) vs v(9)
31 plot v(7) v(9)
32 *print v(9) v(7)
33 .endc
34 .end

```

3.1.2 Simulation results

3.2 Astable Multivibrator

3.2.1 Code snippet

```

1 Astable Multivibrator without diodes
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include zener_B.txt
5
6 .SUBCKT ZENER_12 1 2
7 D1 1 2 DF
8 DZ 3 1 DR
9 VZ 2 3 3.48
10 .MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p VJ=1.00 M
    =0.330
11 + TT=50.1n)
12 .MODEL DR D ( IS=5.49f RS=50 N=1.77 )
13 .ENDS
14
15 *Connections as mentioned in subcircuit file
16 x1 1 2 3 4 5 UA741
17 R1 1 0 30K
18 R2 1 5 35K
19 R4 5 2 50K

```

```

20 C1 2 0 0.01u
21 vcc 3 0 dc 15v
22 vee 4 0 dc -15v
23
24 .tran 0.01m 25m
25 .control
26 run
27 plot v(2) v(5)
28 *print v(5) v(2)
29 .endc
30 .end

```

3.3 Monostable Multivibrator

3.3.1 Code snippet

```

1 Monostable Multivibrator
2 *Including the predefined op-amp subcircuit file
3 .include ua741.txt
4 .include zener_B.txt
5
6 .SUBCKT ZENER_12 1 2
7 D1 1 2 DF
8 DZ 3 1 DR
9 VZ 2 3 3.48
10 .MODEL DF D ( IS=27.5p RS=0.620 N=1.10 CJO=78.3p VJ=1.00 M
    =0.330
11 + TT=50.1n)
12 .MODEL DR D ( IS=5.49f RS=50 N=1.77 )
13 .ENDS
14
15 .SUBCKT button_sw 1 2 c
16 S1 1 2 c 0 b_sw1
17 * Initial value, pulsed value, delay time, rise time, fall
    time, pulse width *
18 V1 c 0 pulse(0 10 0.10 0.0 0.0 100u)
19 .model b_sw1 sw vt=1 vh=0.2 ron=1 roff=1000MEG
20 .ENDS button_sw
21
22 *Connections as mentioned in subcircuit file
23 x1 1 2 3 4 5 UA741
24 R1 1 0 10K
25 R2 1 6 10K
26 R3 6 5 1K
27 R4 2 8 10K
28 C1 2 9 10u

```


```


29 xz1 7 6 ZENER_12
30 xz2 7 0 ZENER_12
31 vcc 3 0 dc 15v
32 vee 4 0 dc -15v
33 vr 8 0 dc 15v
34 vc 9 0 -15v
35
36 xsw 2 9 10 button_sw
37
38 .tran 0.01m 1000m
39 .control
40 run
41 plot v(2) v(6) v(1) v(10)
42 *print v(6) v(2)
43 .endc
44 .end


```

3.3.2 Simulation results


Schimdt Trigger

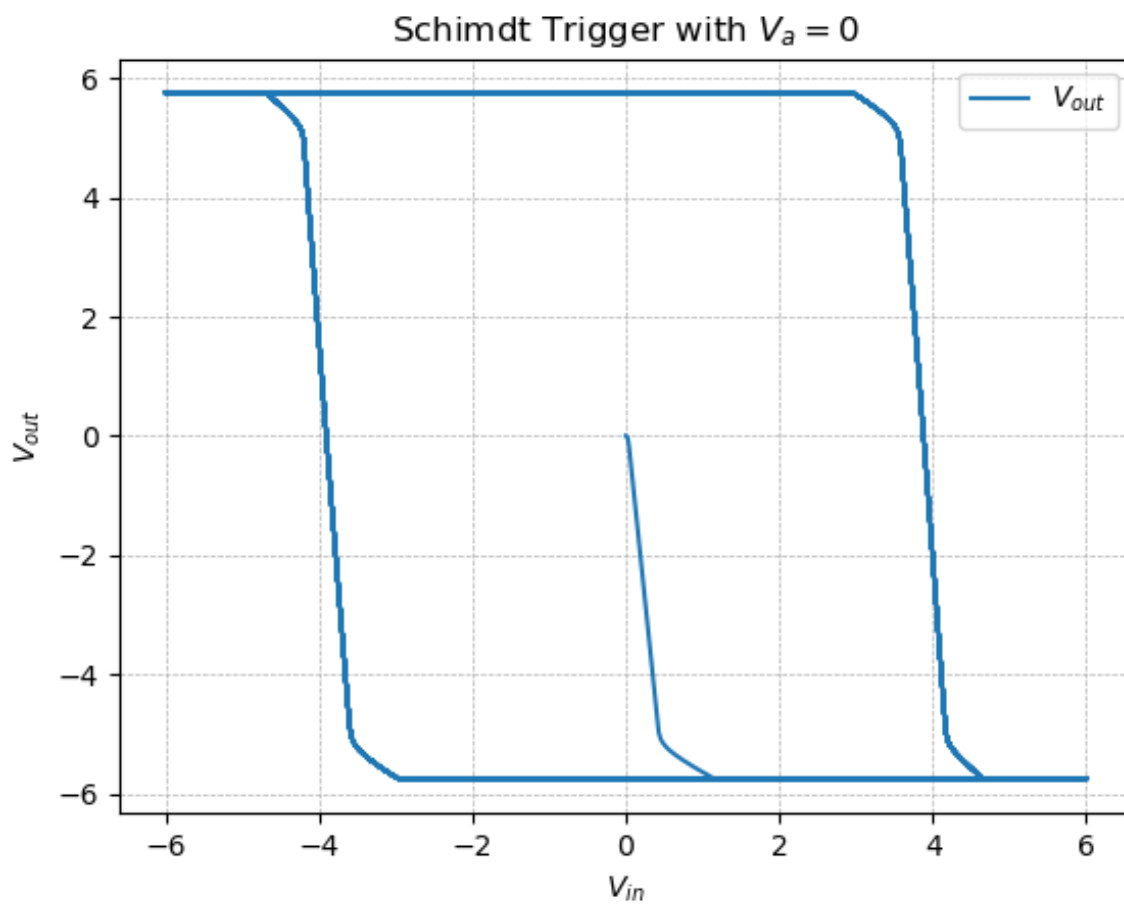


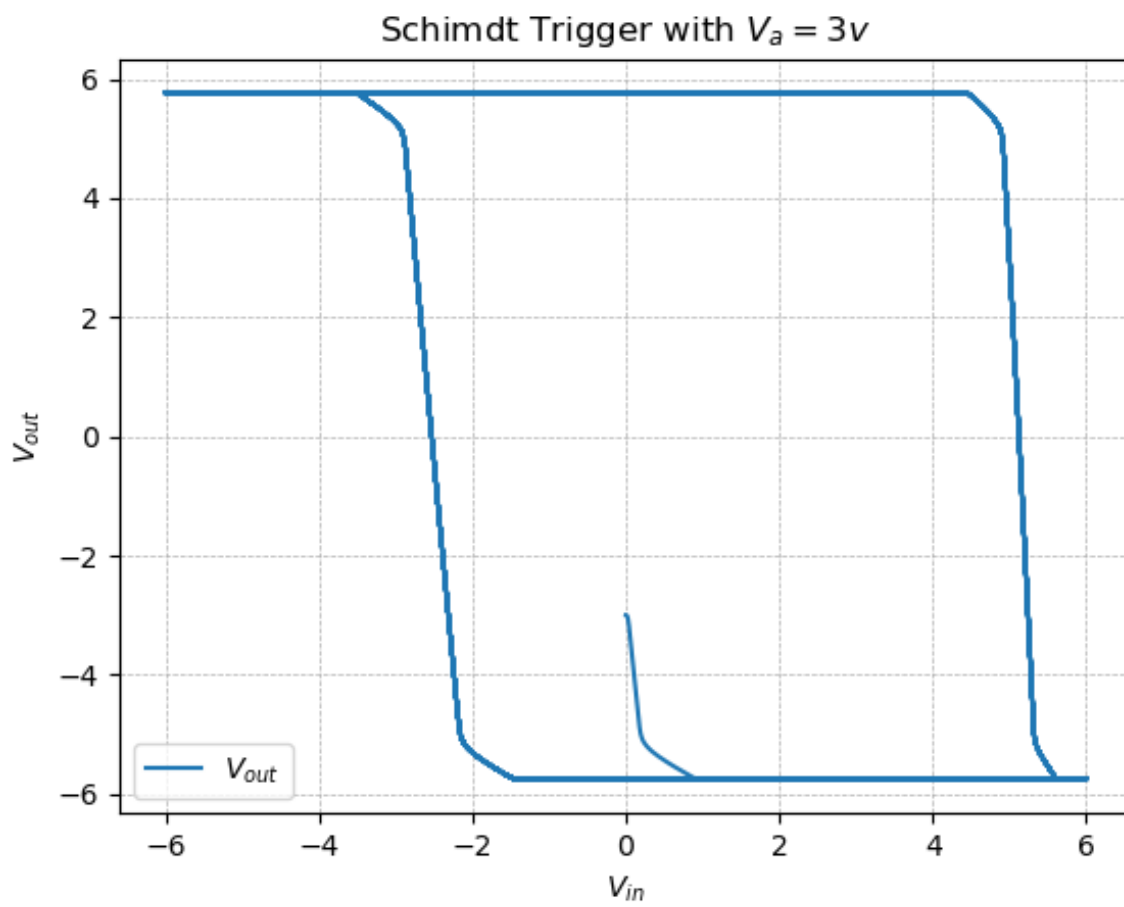

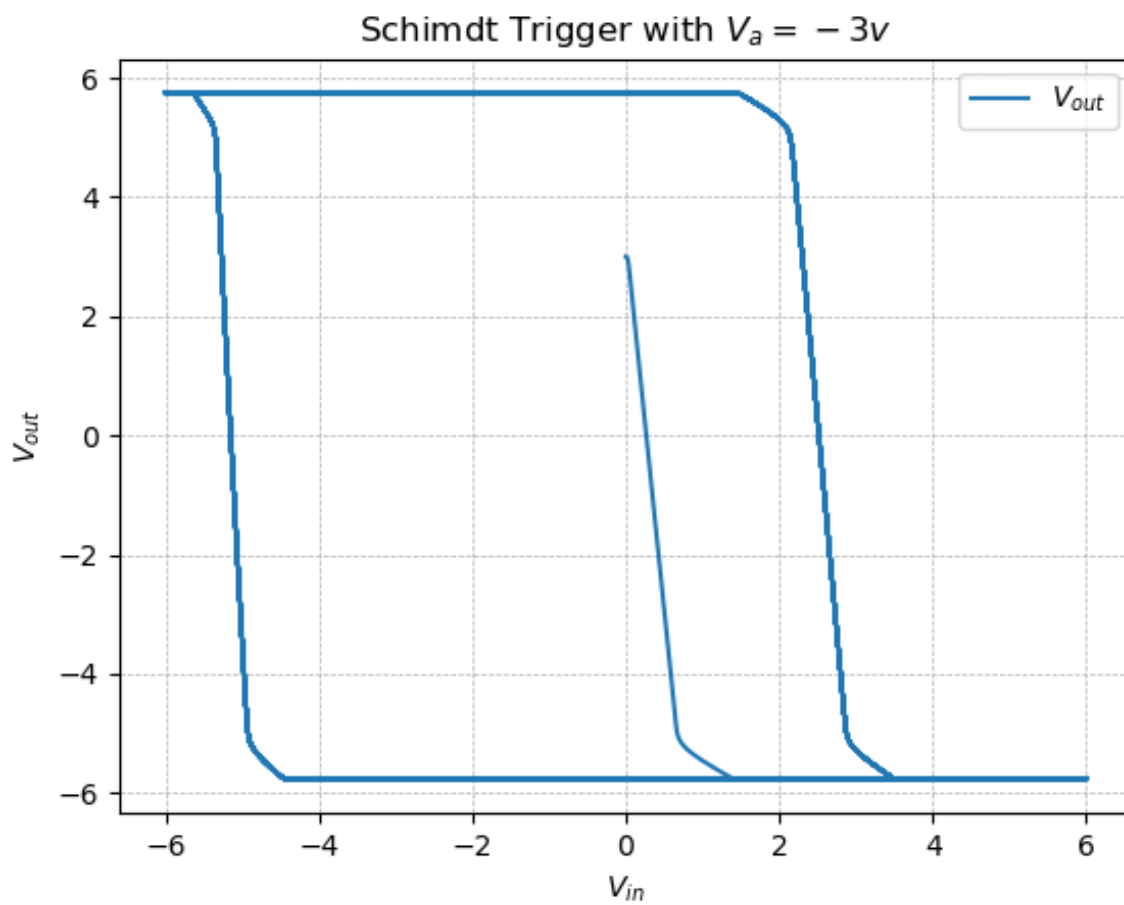


Astable Multivibrator

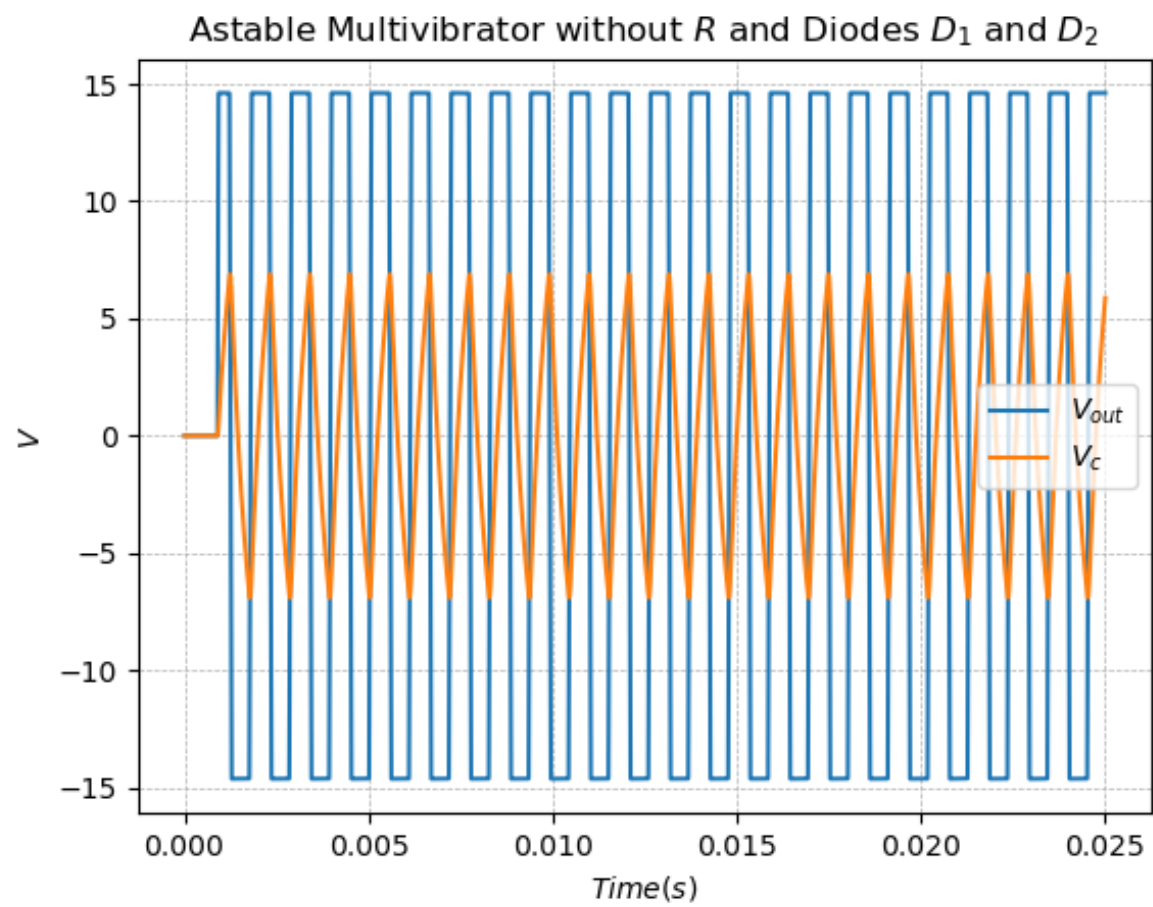

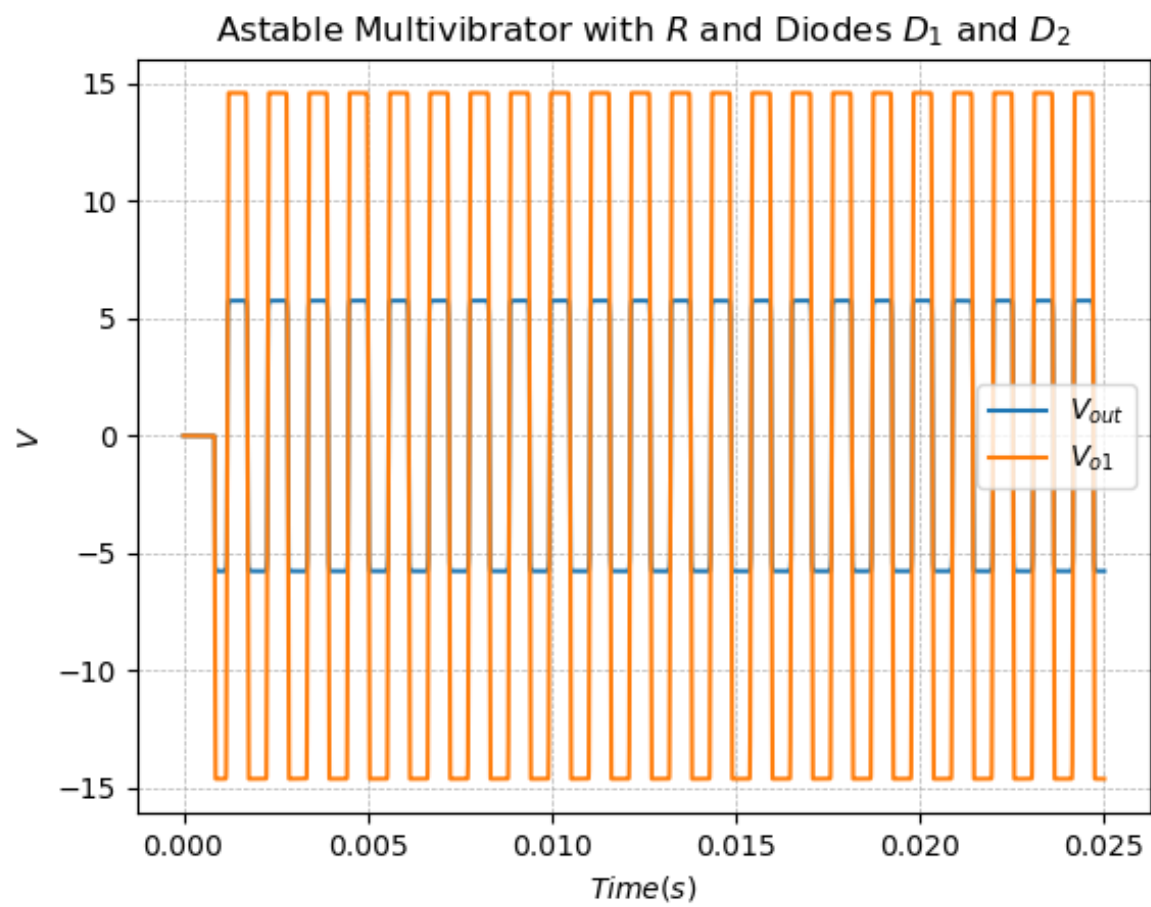

Monostable Multivibrator

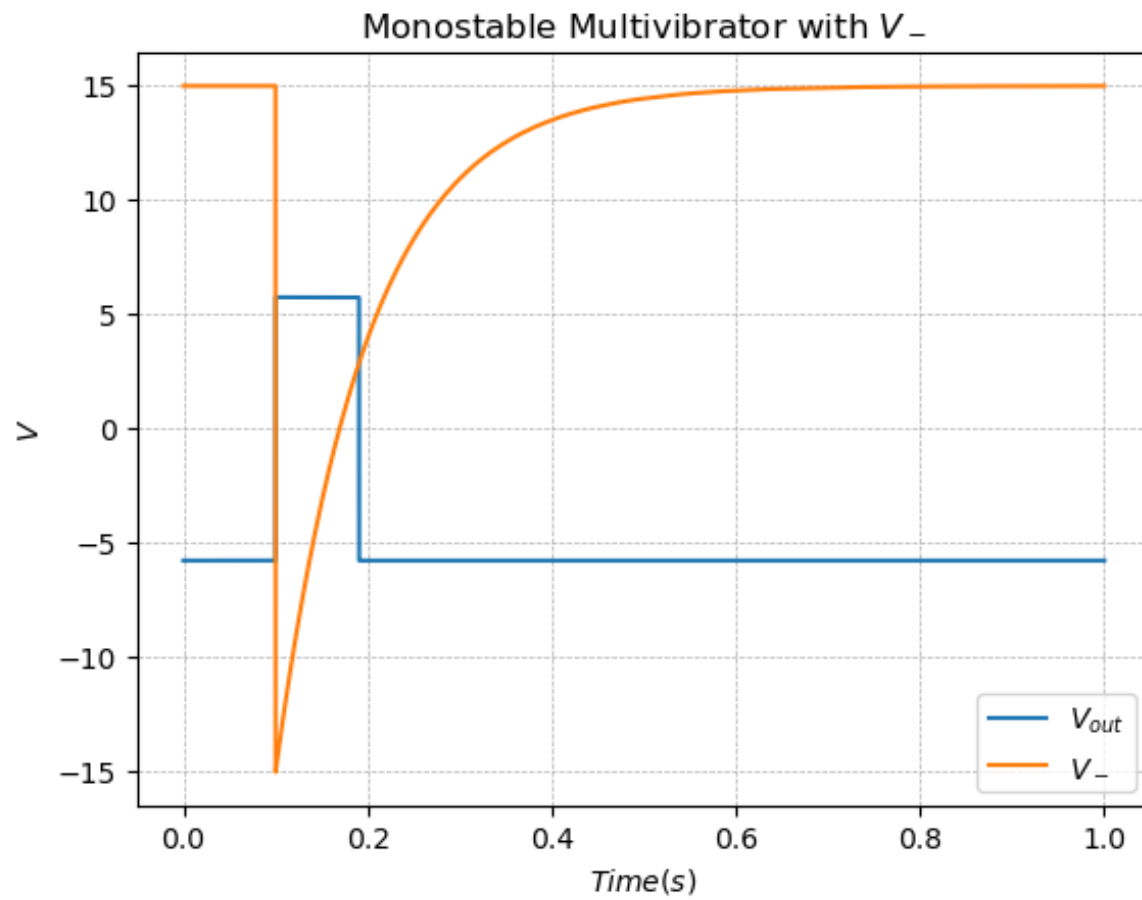

4 Experiment completion status

All the sections were completed